

Unit P5

Electric Circuit

The topics in this unit are:

-  **1 - Static electricity**
-  **2 - Repulsion and attraction**
-  **3 - Electric circuits**
-  **4 - Circuit symbols**
-  **5 - Currents**
-  **6 - Resistance**
-  **7 - Thermistors and light dependent resistors**
-  **8 - Series circuits**
-  **9 - Parallel circuits**
-  **10 - Electromagnetic induction**
-  **11 - Electric Generators**
-  **12 - Power**
-  **13 - Transformers**
-  **14 - Energy**
-  **15 - Cost of electricity**
-  **16 - Efficiency of appliances**

Static Electricity

Some materials that are **insulating** can become **electrically charged** when they are rubbed against each other.

Static builds up when **electrons** are 'rubbed off' one material onto another




The material **receiving** the electrons becomes **negatively** charged and the one **giving up** electrons becomes **positively** charged

Repulsion and Attraction

[Next page](#)

When two **charged** materials are held close together they exert a **force** on each other.

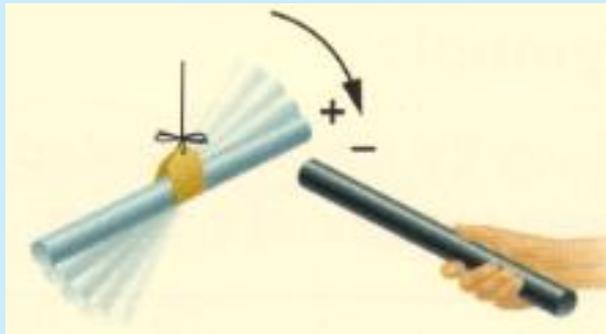If two **identical** charges are held together, they **repel** each other



If two **opposite** charges are held together, they **attract** each other


[Main menu](#)

Electric Circuits

In an electric circuit, an **electric current** flows through.

A current is a **flow of charges**.

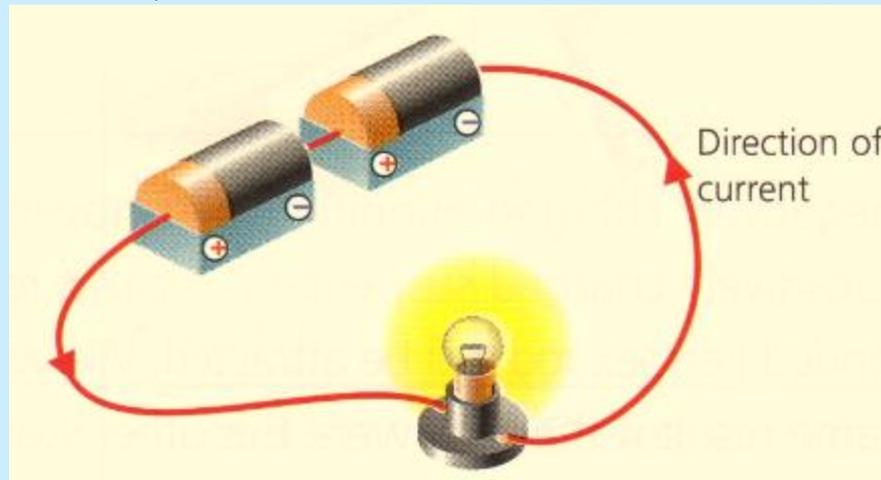The battery causes the charges to move in a **continuous loop** around wires and components




In **metal** conductors, there are lots of charges **free** to move.

Circuit Symbols

Components can be represented using circuit symbols



cell

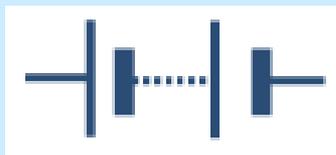

battery



bulb




ammeter



switch




voltmeter

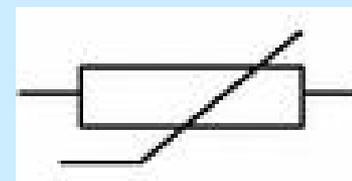


thermistor



resistor

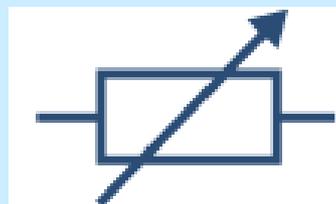

variable resistor

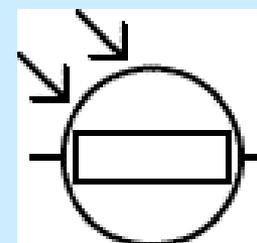

light dependent resistor

Currents

A current is the **flow of charge** around a circuit

A **direct** current (d.c.) always flows in the **same direction**

An **alternating** current (a.c.) changes the direction of **flow back and forth**

The amount of current flowing in a circuit depends on the **potential difference** across the components

The **greater** the potential difference (**voltage**), the greater the current that flows through the component.

Resistance

[Next page](#)



Components, such as lamps, resist the flow of charge through them. They have **resistance**.

The **greater** the resistance of a component, the **smaller** the current that flows.

Resistance (**ohms**, Ω) measures how hard it is to get a current through.

It can be calculated by

$$\text{Resistance } (\Omega) = \frac{\text{voltage (V)}}{\text{current (A)}}$$

[Main menu](#)

Thermistors and Light Dependent Resistors



[Next page](#)

The resistance of some materials depends on other conditions

Thermistors

The resistance of a **thermistor** depends on its **temperature**.

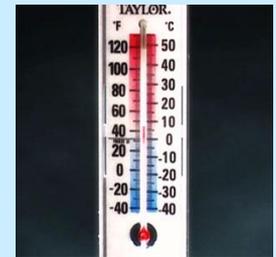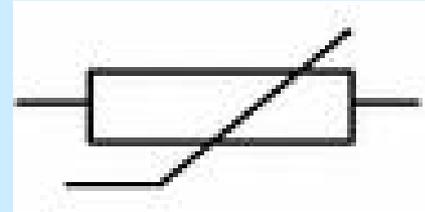
As the temperature **increases**, the resistance **decreases** allowing more current to flow.



Light Dependent Resistor

The resistance of an LDR depends on the **light intensity**.

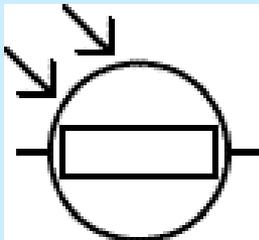As the amount of light **increases**, the resistance **decreases** allowing more current to flow



[Main menu](#)

Series Circuits


In a **series circuit** all the components are connected in **one loop**.

The current flowing through each component is the same

$$A_1 = A_2 = A_3$$

The potential difference (voltage) across the components is the same as the potential difference across the battery

$$V_1 = V_2 + V_3$$

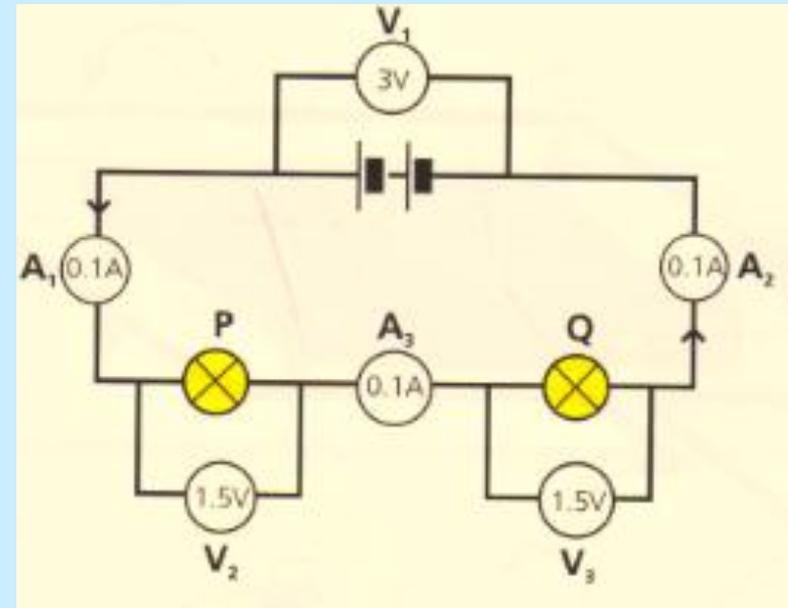

If a circuit has 2 **identical** components they will have the **same** voltage across them.


If the components are **different** the one with the **greatest** resistance will have the **greatest** voltage

Parallel Circuits

The components in a parallel circuit are connected in separate loops.

The total current going from and back to the battery is the same

$$A_1 = A_2 + A_3 = A_4$$

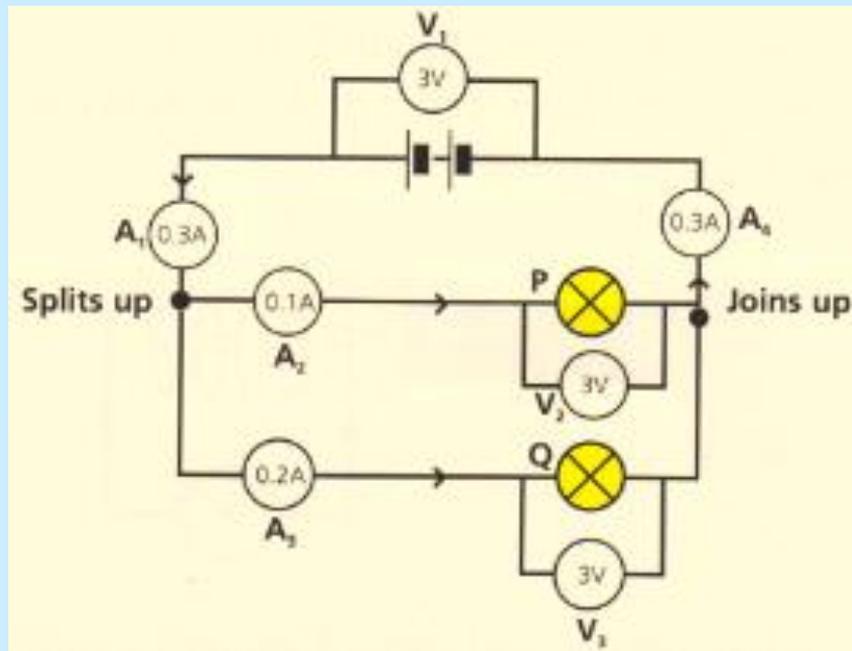


The amount of current going through each component depends on the resistance.

The greater the resistance the smaller the current.

The current is smallest through the component with the largest resistance

Electromagnetic Induction


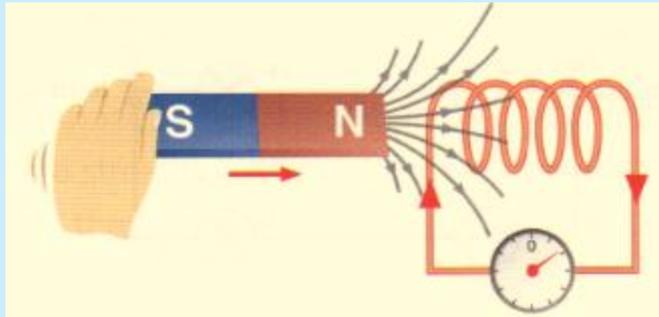
In electromagnetic induction, **movement** produces current.



If a wire cuts through the magnetic field, then a **voltage** is induced.


Moving the magnet into the coil **induces** a current in one direction

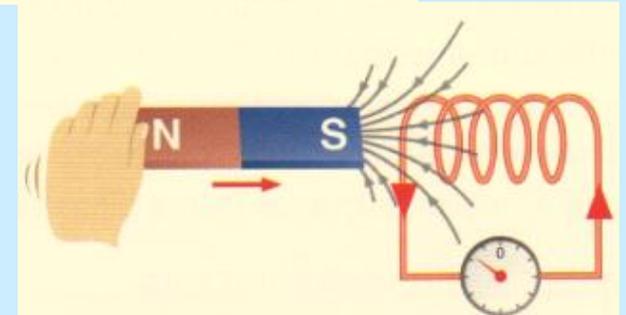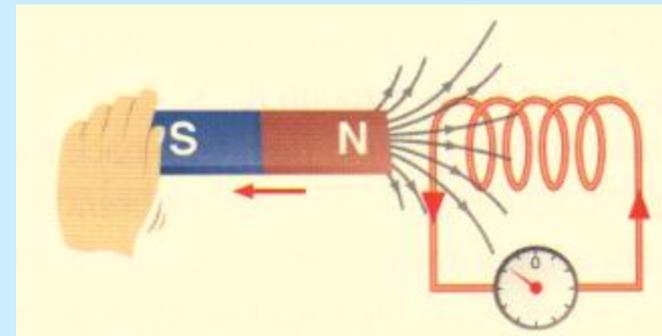We can make a current in the **opposite** direction by moving the magnet **out of the coil** or moving the other **pole** of the magnet into the coil



Electric Generators

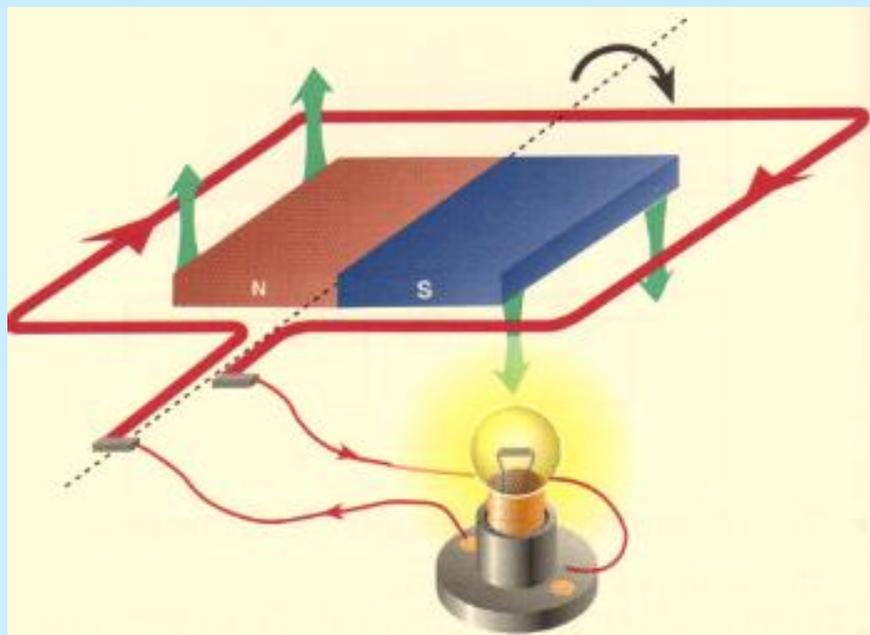Generators use **electromagnetic induction** to generate electricity by **rotating** a magnet inside a coil.



The size of the voltage can be increased by:

1. Increasing the **speed of rotation**
2. Increasing the **strength** of the magnetic field
3. Increasing the number of **turns**
4. Putting an **iron core** inside the coils

Power

Power, measured in **Watts**, is a measure of how much **energy** is transferred every **second**

$$\text{power (W)} = \text{potential difference (V)} \times \text{current (A)}$$

Example


An electric motor works at a current of 3A and a potential difference of 24V. What is the power of the motor?

$$\begin{aligned}\text{Power} &= 24\text{V} \times 3\text{A} \\ &= 72\text{ W}\end{aligned}$$

Transformers

Transformers are used to change the **voltage** of an **alternating current**.

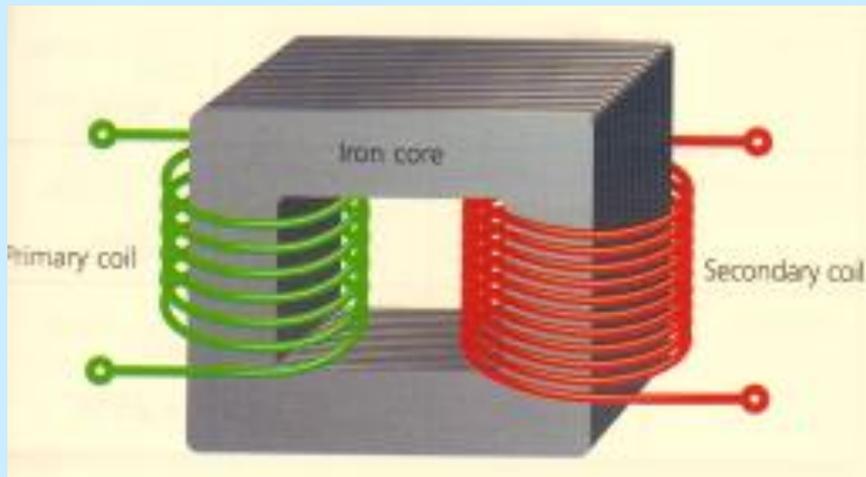A transformer consists of **2 coils**, called **primary** and **secondary** coils wrapped around an **iron core**.



When two coils are close together a changing magnetic field in one coil can generate a **voltage** in the other current.

Energy

Energy is measured in **Joules (J)**.

Domestic electricity is measured in **kilowatt hours (kWh)**

The amount of energy transferred can be calculated by:

$$\text{energy transferred (J)} = \text{power (W)} \times \text{time (s)}$$

$$\text{energy transferred (kWh)} = \text{power (kW)} \times \text{time (h)}$$

Cost of Electricity

If we know the **power**, **time** and **cost per kilowatt hour**, we can calculate the **cost of energy**.

$$\text{total cost} = \text{number of units (kWh)} \times \text{cost per unit}$$

Example

A 2000W electric fire is switched on for 30 minutes. How much does it cost if electricity is 8p per unit?



$$\begin{aligned} \text{energy} &= 2\text{kW} \times 0.5 \text{ h} \\ &= 1\text{kWh} \end{aligned}$$

$$\begin{aligned} \text{cost} &= 1\text{kWh} \times 8\text{p} \\ &= 8\text{p} \end{aligned}$$

Efficiency of Appliances

The greater the amount of energy that is usefully transferred, the more efficient the appliance is.

It is calculated by:

$$\text{Efficiency (\%)} = \frac{\text{energy usefully transferred}}{\text{total energy}} \times 100$$

Appliance	Energy in	Useful energy out	Efficiency
Light bulb	100 J/s	Light: 20 J/s	$20/100 \times 100$ = 20%
Kettle	2000 J/s	Heat: 1800 J/s	$1800/2000 \times 100$ = 90%
Electric motor	500 J/s	Kinetic: 300 J/s	$300/500 \times 100$ = 60%
Television	200 J/s	Light: 20 J/s Sound: 30 J/s	$50/200 \times 100$ = 25%